

Design of a Simple CS Amplifier

Emmanuel Jesus R. Estallo
Electrical and Electronics Engineering Institute
University of the Philippines - Diliman
Quezon City, Philippines
emmanuel.estallo@eee.upd.edu.ph

I. CS AMPLIFIER

The desired specs are as follows:

- $|A_v| > 40$ at $V_{DS} = V_{DD}/2 = 0.9V$
- Output swing: $400mV$
- Unity-gain frequency: $f_u = 100MHz$, $C_L = 5pF$
- $V^* = 200mV$

A. Selecting I_D

The transconductance can be obtained from:

$$g_m = 2\pi f_u C_L$$

this gives us

$$g_m = 3.14 mS$$

The current can be obtained from:

$$V^* = 2 \cdot \left(\frac{g_m}{I_D} \right)^{-1}$$

and a V^* of $200 mV$ corresponds to a g_m/I_D of 10.

Thus,

$$I_D = 314 \mu A$$

B. Choosing the length

To find the appropriate length, I did a DC sweep on VGS and checked if the intrinsic gain at V^* is > 40 .

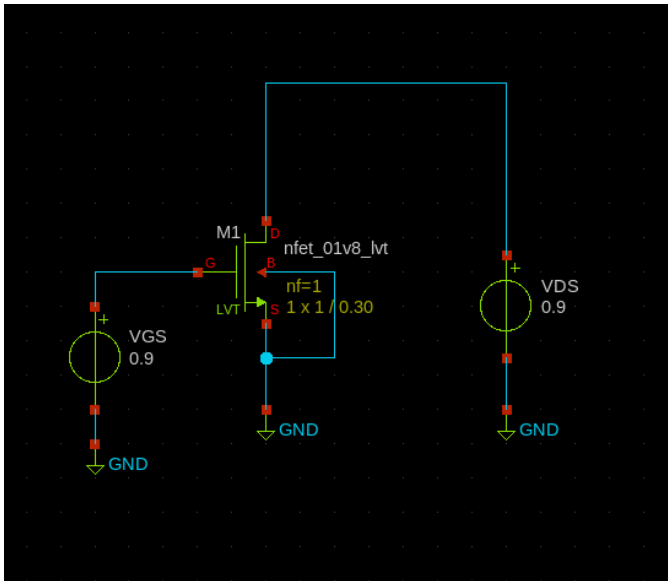


Fig. 1. Schematic diagram

At the minimum length, the intrinsic gain is lower than what is desired. We select $L = 0.30\mu m$ since it satisfies the specifications. $L = 0.25\mu m$ also meets the specifications, however, for a greater swing, the larger length is selected.

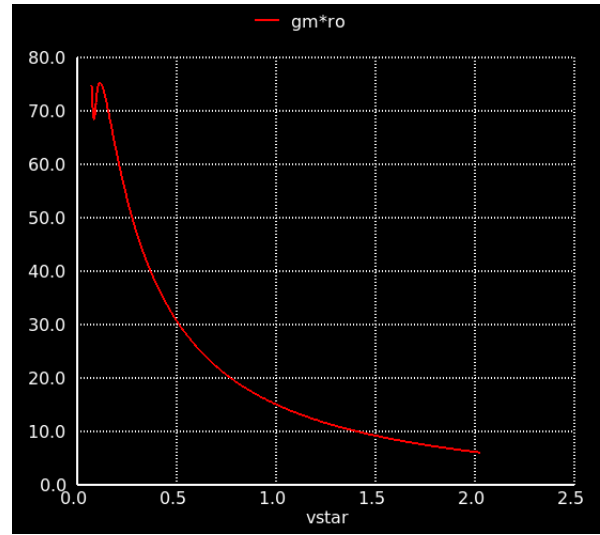


Fig. 2. Intrinsic gain

The V^* vs I_D plot for a transistor with $W = 1\mu m$, $L = 0.30\mu m$ is shown below.

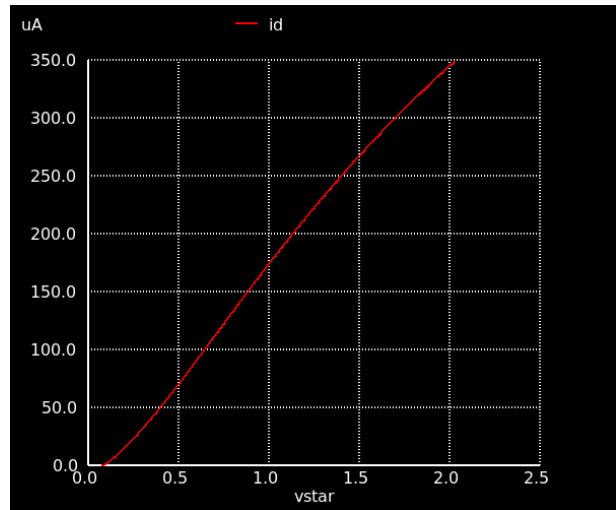


Fig. 3. I_D vs V^* , $W = 1\mu m$

C. Scaling the width

A python script is used to calculate the scale factor k_W to achieve the required I_D . The width is scaled using k_W . Multiplying the width by k_W scales I_D by approximately the same factor. For this activity, $k_W = 21$. To check, a MEAS directive is used. The required current is $I_D = 314\mu A$, what we got after scaling the width is $345\mu A$, which is quite close.

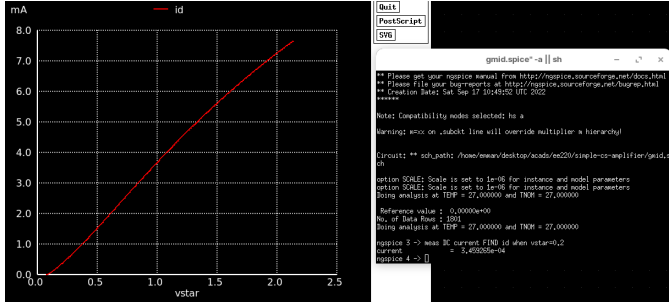


Fig. 4. I_D vs V^* , $W = 21\mu m$

D. Output and input swing

E. AC analysis

The circuit that is used to get the magnitude response is shown below.

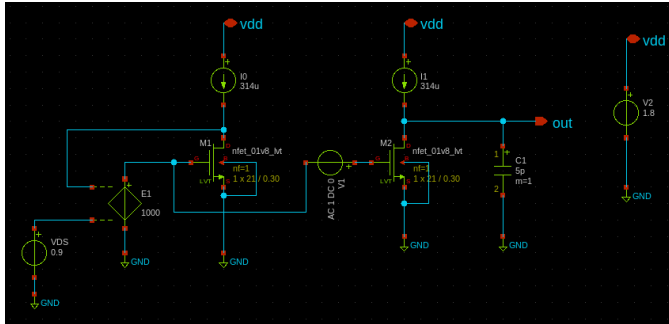


Fig. 5. Schematic

An AC sweep from $1Hz$ to $1GHz$ is used to obtain Fig. 6. Using a MEAS directive, $f_u = 104MHz$ which is close to our desired f_u . At low frequencies, the gain is $\approx 35dB$ which is $\approx 60 V/V$

 


Fig. 6. Magnitude response