

Activity 8: Noise Analysis

Emmanuel Jesus R. Estallo
Electrical and Electronics Engineering Institute
University of the Philippines - Diliman
Quezon City, Philippines
emmanuel.estallo@eee.upd.edu.ph

I. TRANSISTOR NOISE

A. NMOS Noise

For the NMOS with $V_{DS} = V_{GS} = 900\text{mV}$, $I_D = 439\mu\text{A}$. Additionally, $g_m = 2.44\text{mS}$ and $v^* = 440\text{mV}$ as seen in the image below.

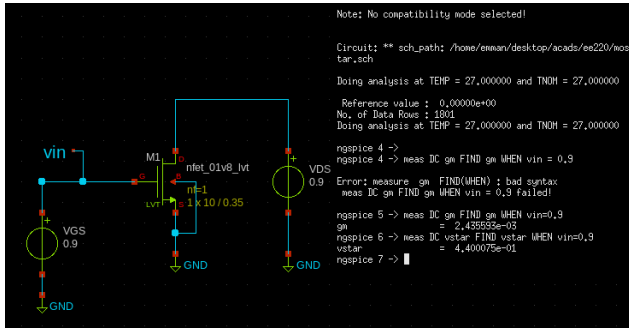


Fig. 1. g_m and v^*

The values are obtained by using the MEAS command. Note that the TT corner is used.

1) *Simulations*: Flicker noise dominates the range $f < 500\text{MHz}$ whereas thermal noise dominates the region where $f > 500\text{MHz}$. With this, the flicker noise corner is at around $f = 500\text{MHz}$.

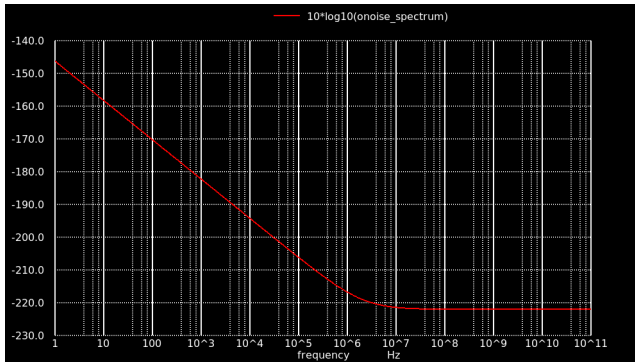


Fig. 2. Output Noise PSD

2) *Estimating γ* : Recall that in the absence of flicker noise, and assuming $\alpha = 1$

$$\overline{i_{od}^2} = 4kT\gamma g_m$$

The total integrated noise power is equal to

$$\begin{aligned} P_{i,noise} &= \int_{f_1}^{f_2} \overline{i_{od}^2} df \\ &= \int_{f_1}^{f_2} 4kT\gamma g_m df \\ &= 4kT\gamma g_m \cdot (f_2 - f_1) \end{aligned}$$

This means that if the integrated output noise power is obtained at the region where thermal noise is dominant, it is possible to directly compute for γ . To estimate, the total output noise power with 1-GHz bandwidth centered at around 90-GHz will be chosen. Since

B. PMOS Noise