

# Design of a Simple CS Amplifier

Emmanuel Jesus R. Estallo  
Electrical and Electronics Engineering Institute  
University of the Philippines - Diliman  
Quezon City, Philippines  
emmanuel.estallo@eee.upd.edu.ph

## I. CS AMPLIFIER

The desired specs are as follows:

- $|A_v| > 40$  at  $V_{DS} = V_{DD}/2 = 0.9V$
- Output swing:  $400mV$
- Unity-gain frequency:  $f_u = 100MHz$ ,  $C_L = 5pF$
- $V^* = 200mV$

The transconductance can be obtained from:

$$g_m = 2\pi f_u C_L$$

this gives us

$$g_m = 3.14 mS$$

The current can be obtained from:

$$V^* = 2 \cdot \left( \frac{g_m}{I_D} \right)^{-1}$$

and a  $V^*$  of  $200 mV$  corresponds to a  $g_m/I_D$  of 10.

Thus,

$$I_D = 314 \mu A$$

The  $V^*$  vs  $I_D$  plot for a transistor with  $W = 1\mu m$ ,  $L = 0.30\mu m$  is shown below.

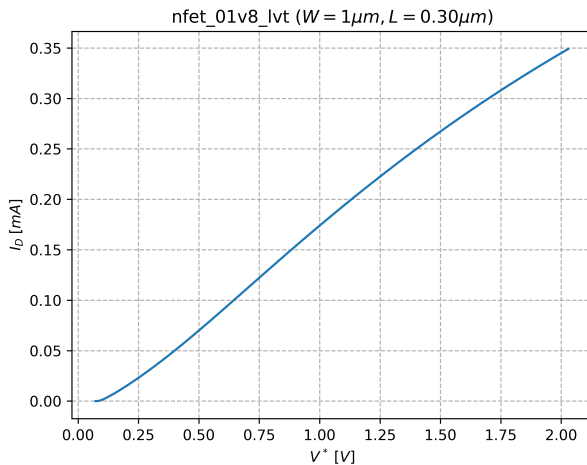


Fig. 1.  $I_D$  vs  $V^*$

To get the desired  $I_D$ , the width should be multiplied by 21.