

# Design of a Simple CS Amplifier

Emmanuel Jesus R. Estallo  
Electrical and Electronics Engineering Institute  
University of the Philippines - Diliman  
Quezon City, Philippines  
emmanuel.estallo@eee.upd.edu.ph

## I. CS AMPLIFIER

The desired specs are as follows:

- $|A_v| > 40$  at  $V_{DS} = V_{DD}/2 = 0.9V$
- Output swing:  $400mV$
- Unity-gain frequency:  $f_u = 100MHz$ ,  $C_L = 5pF$
- $V^* = 200mV$

### A. Selecting $I_D$

The transconductance can be obtained from:

$$g_m = 2\pi f_u C_L$$

this gives us

$$g_m = 3.14 mS$$

The current can be obtained from:

$$V^* = 2 \cdot \left( \frac{g_m}{I_D} \right)^{-1}$$

and a  $V^*$  of  $200 mV$  corresponds to a  $g_m/I_D$  of 10.

Thus,

$$I_D = 314 \mu A$$

### B. Choosing the length

To find the appropriate length, I did a DC sweep on VGS and checked if the intrinsic gain at  $V^*$  is  $> 40$ .

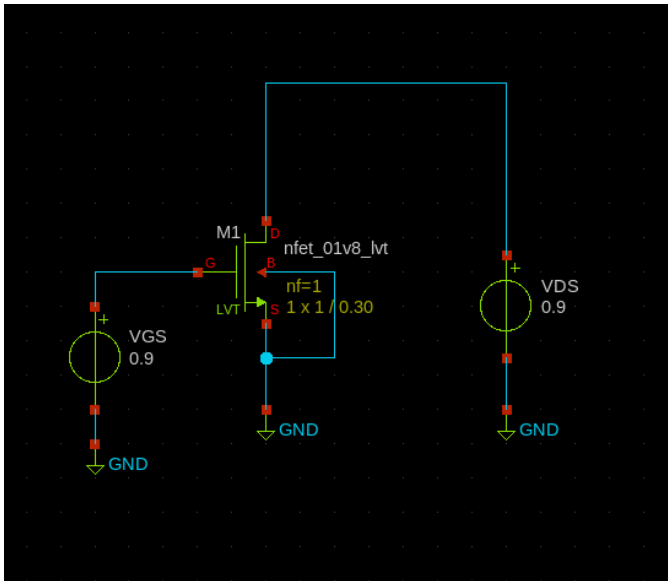


Fig. 1. Schematic diagram

At the minimum length, the intrinsic gain is lower than what is desired. We select  $L = 0.30\mu m$  since it satisfies the specifications.  $L = 0.25\mu m$  also meets the specifications, however, for a greater swing, the larger length is selected.

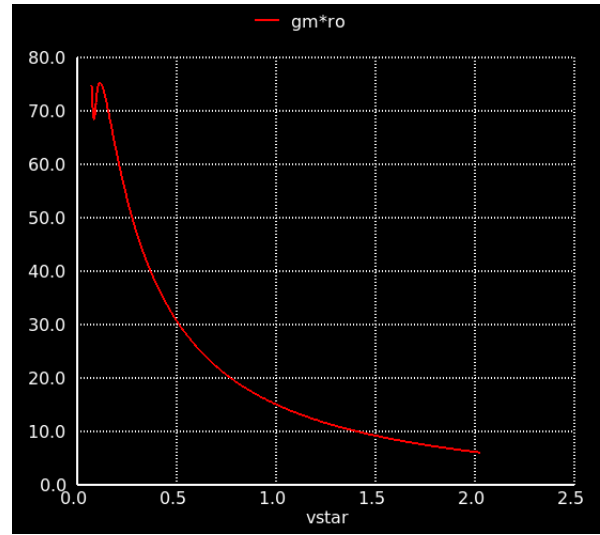


Fig. 2. Intrinsic gain

The  $V^*$  vs  $I_D$  plot for a transistor with  $W = 1\mu m$ ,  $L = 0.30\mu m$  is shown below.

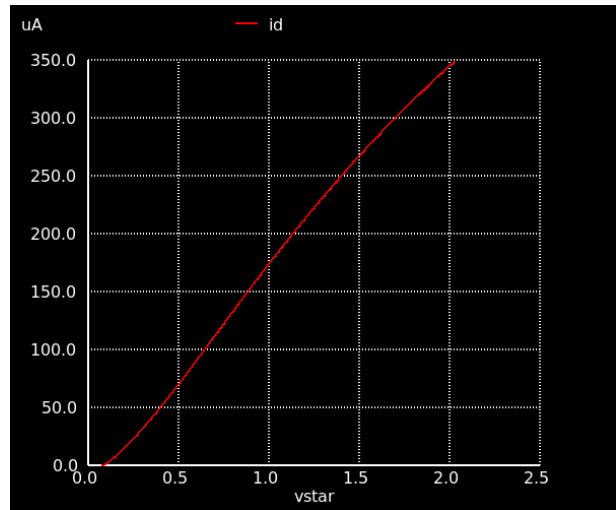


Fig. 3.  $I_D$  vs  $V^*$ ,  $W = 1\mu m$

### C. Scaling the width

A python script is used to calculate the scale factor  $k_W$  to achieve the required  $I_D$ . The width is multiplied to the scaling factor. This also scales  $I_D$ . For this activity,  $k_W = 21$ . To check, a MEAS directive is used.

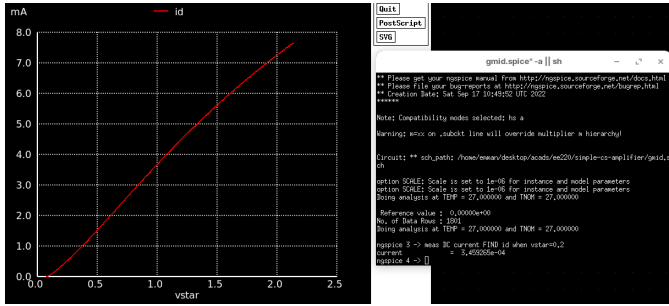


Fig. 4.  $I_D$  vs  $V^*$ ,  $W = 21\mu m$